

# ASSEMBLY ASSIGNMENT

Koushik Kalyani

koushikkalyani369@gmail.com


IITH - Future Wireless Communication

# CONTENTS

<b>I</b>	<b>Question</b>	1
<b>II</b>	<b>Answer</b>	1
	II-A Truth Table . . . . .	1
	II-B K-Map Implentation . . . . .	1
<b>III</b>	<b>Components</b>	2
<b>IV</b>	<b>Implementation</b>	2

## I. QUESTION

The digital circuit shown \_\_\_\_\_

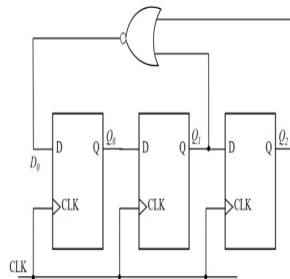

## II. ANSWER

The above question can be solved by using Truth Table and karnaugh-map.

### A. Truth Table

Present State			Flip-Flop i/p			Next State		
$Q_0$	$Q_1$	$Q_2$	$D_0$	$D_1$	$D_2$	$Q'_0$	$Q'_1$	$Q'_2$
0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	1	1	0
1	1	0	0	1	1	0	1	1
0	1	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

Therefore, given circuit is Divide by 5 circuit.

### B. K-Map Implementation

$$Q_1 Q_2$$

		00	01	11	10
$Q_0$	0	1	0	0	0
	1	1	0	0	0

$$D_0 = \overline{Q}_1 \cdot \overline{Q}_2$$

$$Q_1 Q_2$$

		00	01	11	10
$Q_0$	0	0	0	0	0
	1	1	0	0	1

$$D_1 = Q_0 \cdot \overline{Q}_2$$

$$Q_1 Q_2$$

		00	01	11	10
$Q_0$	0	0	0	1	0
	1	0	0	0	1

$$D_2 = \overline{Q}_0 \cdot Q_1 \cdot Q_2 + Q_0 \cdot Q_1 \cdot \overline{Q}_2$$

### III. COMPONENTS

Components	Values	Quantity
Arduino	Uno	1
Jumper Wires	M-M	25
Breadboard		1
LED		3
Resistor	$\geq 220\Omega$	3
Flip Flop	7474	2

### IV. IMPLEMENTATION

	INPUT			OUTPUT			CLOCK		5V			
	Q0	Q1	Q2	Q0'	Q1'	Q2'	A5					
Arduino	D9	D10	D11	D2	D3	D4	A5					
7474	5	9		2	12		CLK1	CLK2	1	4	10	13
7474			9			12	CLK1	CLK2	1	4	10	13

Connections

#### Procedure

1. Connect the circuit as per the above table.
2. Connect LEDs to the output pins of the Arduino to see output.
3. Execute the circuit using the below code.

<https://github.com/koushikkalyani/FWC/blob/main/Assembly/assembly.asm>

4. Visit for video demonstration .

<https://github.com/koushikkalyani/FWC/blob/main/Assembly/AssemblyDemo.mp4>