

ASSEMBLY ASSIGNMENT

Koushik Kalyani
koushikkalyani369@gmail.com
IITH - Future Wireless Communication

CONTENTS


I	Question	1
II	Answer	1
	II-A Truth Table	1
	II-B K-Map Implementation	1
III	Components	2
IV	Implementation	2

B. K-Map Implementation

		$Q_1 Q_2$			
		00	01	11	10
Q_0	0	1	0	0	0
	1	1	0	0	0

I. QUESTION

The digital circuit shown _____

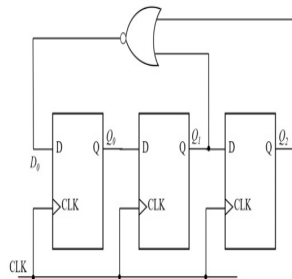

$$D_0 = \overline{Q_1} \cdot \overline{Q_2}$$

		$Q_1 Q_2$			
		00	01	11	10
Q_0	0	0	0	0	0
	1	1	0	0	1

II. ANSWER

The above question can be solved by using Truth Table and karnaugh-map.

A. Truth Table

Present State			Flip-Flop i/p			Next State		
Q_0	Q_1	Q_2	D_0	D_1	D_2	Q'_0	Q'_1	Q'_2
0	0	0	1	0	0	1	0	0
1	0	0	1	1	0	1	1	0
1	1	0	0	1	1	0	1	1
0	1	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

$$D_1 = Q_0 \cdot \overline{Q_2}$$

		$Q_1 Q_2$			
		00	01	11	10
Q_0	0	0	0	1	0
	1	0	0	0	1

$$D_2 = \overline{Q_0} \cdot Q_1 \cdot Q_2 + Q_0 \cdot Q_1 \cdot \overline{Q_2}$$

Therefore, given circuit is Divide by 5 circuit.

III. COMPONENTS

Components	Values	Quantity
Arduino	Uno	1
Jumper Wires	M-M	25
Breadboard		1
LED		3
Resistor	$\geq 220\Omega$	3
Flip Flop	7474	2

IV. IMPLEMENTATION

	INPUT			OUTPUT			CLOCK		5V			
	Q0	Q1	Q2	Q0'	Q1'	Q2'	A5					
Arduino	D9	D10	D11	D2	D3	D4	A5					
7474	5	9		2	12		CLK1	CLK2	1	4	10	13
7474			9			12	CLK1	CLK2	1	4	10	13

Connections

Procedure

1. Connect the circuit as per the above table.
2. Connect LEDs to the output pins of the Arduino to see output.
3. Execute the circuit using the below code.

<https://github.com/koushikkalyani/FWC/blob/main/Assembly/assembly.asm>

4. Visit for video demonstration .

<https://github.com/koushikkalyani/FWC/blob/main/Assembly/AssemblyDemo.mp4>